

MORADABAD INSTITUTE OF TECHNOLOGY, MORADABAD
ELECTRICAL ENGINEERING DEPARTMENT

Class Test-1 (Session 2025-26) (SET-1)

Course: B. Tech

Subject: Fundamentals of Electrical Engineering

Subject Code: BEE-101

Semester: Ist

Section: E, F, G, H

Time: 60 Minutes

Max. Marks: 20

S. No.	1	2	3	4	5	6
CO No.	CO2	CO2	CO2	CO1	CO1	CO3
Bloom's Level	K1	K3	K2	K3	K3	K2

Note: 1) This paper contains three sections, Section (A) (B) & (C)

2) All sections are compulsory

Section (A)

Attempt this question. This question carries 2 marks.

(1*2 = 2)

- 1) Derive expression for resonant frequency in series R-L-C circuit.

Section (B)


Attempt all questions. Each question carries 3 marks.

(2*3 = 6)

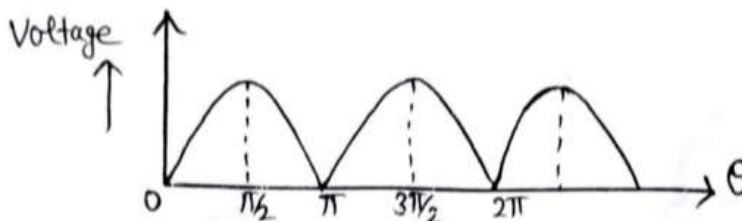- 2) An alternating voltage is given by $v = 141.4 \sin 314 t$. Find (i) the instantaneous value of voltage when 't' is 3 ms (ii) the time taken for the voltage to reach 100 V for the first time after passing through zero value.

OR

Find rms average value and peak factor of the voltage waveform shown in figure.



- 3) For an ac circuit $v = 200 \sin 377 t$ volts, and $i = 9 \sin (377 t - 30^\circ)$ amperes. Determine true power, apparent power and reactive power of circuit.

OR


Show that the average power for purely inductive circuit is zero.

Section (C)


Attempt all questions. Each question carries 4 marks.

(3*4 = 12)

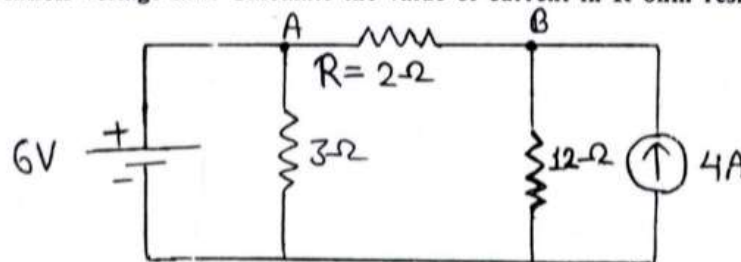- 4) State Kirchhoff voltage law. Calculate the value of current in R ohm resistance by using mesh analysis method.



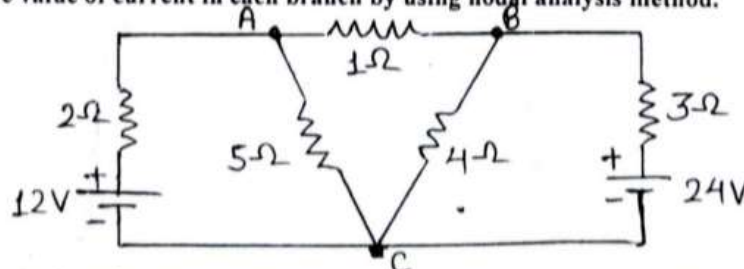- 5) Define with examples (i) Unilateral and Bilateral Elements.
(ii) Determine the value of current in each branch by using nodal analysis method.



- 6) (i) Give the names (write only names) of different types of magnetic materials with examples.
(ii) Derive emf equation of normal two winding transformer.

approved

Saurabh
08/10/25

MORADABAD INSTITUTE OF TECHNOLOGY, MORADABAD
ELECTRICAL ENGINEERING DEPARTMENT
Class Test-1 (Session 2024-25) (SET-1)

Course: B. Tech

Subject: Fundamentals of Electrical Engineering

Subject Code: BEE-201

Semester: 1st

Section: A, B, C, D

Time: 60 Minutes

Max. Marks: 20

S. No.	1	2	3	4	5	6
CO No.	CO3	CO2	CO2	CO1	CO1	CO2
Bloom's Level	K1	K2	K3	K3	K3	K4

Note: 1) This paper contains three sections, Section (A) (B) & (C)

2) All sections are compulsory

Section (A)

(1*2 = 2)

Attempt this question. This question carries 2 marks.

- 1) With the help of examples classified different types of magnetic materials.

Section (B)

(2*3 = 6)


Attempt all questions. Each question carries 3 marks.

- 2) Derive an expression for form factor and peak factor for sinusoidal voltage.

OR

Find rms, average value and peak factor of the voltage waveform shown in figure.

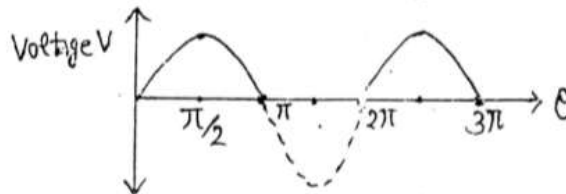Peak factor = $\frac{\text{max}}{\text{rms}}$



- 3) The voltage applied to a circuit is $v = 100 \sin(\omega t + 30^\circ)$ & current flowing in the circuit is $i = 20 \sin(\omega t + 60^\circ)$. Determine the impedance, resistance, reactance, power and power factor of the circuit.

OR


An alternating voltage is given by $v = 141.4 \sin 314 t$. Find (i) frequency (ii) rms value (iii) average value (iv) the instantaneous value of voltage when 't' is 2 ms (v) the time taken for the voltage to reach 100 V for the first time after passing through zero value.

Section (C)

(3*4 = 12)


Attempt all questions. Each question carries 4 marks.

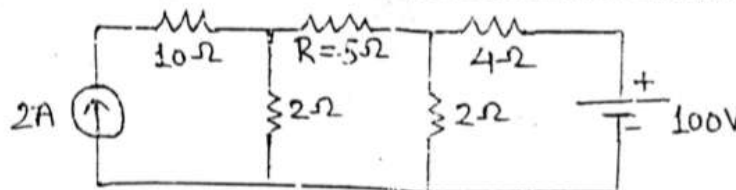- 4) (a) Define with examples (i) Unilateral and Bilateral Elements (ii) Active and Passive Elements
 (b) State Kirchhoff voltage law. Calculate the value of current in R ohm resistance by using mesh analysis method.



Resistor network circuit

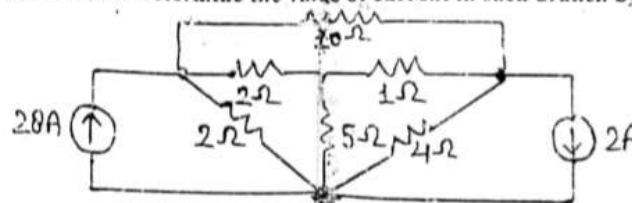- 5) State Kirchhoff current law. Determine the value of current in each branch by using nodal analysis method.



- 6) Define the term Resonance. Derive expression for resonant frequency in series R-L-C circuit. Also draw resonance curve.

For any query contact to: Mr. Saurabh Saxena 789504313, Mr. Akash Kr. Gautam 8954751891, Mr. Lalit Pareekha 7060460472

Approved
 Saurabh
 17-05-25